

# **Sine wave generator project**

## **Electrical department**

### **First year**

### **section:2**

#### **Project made by:**

**omar mohsen emam                      2017015**

**ali mohamed ali                        2017080**

**omar abdelmeniem                    2017156**

## **SEVEN WAYS TO GENERATE A SINE WAVE:**

- 1- WIEN BRIDGE OSCILLATOR.
- 2-PHASE-SHIFT OSCILLATOR.
- 3-COLPITTS CRYSTAL OSCILLATOR.
- 4-SQUARE WAVE AND FILTER.
- 5-DIRECT DIGITAL SYNTHESIS.
- 6-FUNCTION GENERATOR.
- 7-PULSE-BASED SINE WAVE GENERATORS.

## **SQUARE WAVE AND FILTER:**

### **\*Tools:**

- 1- Ic 555 ( CMOS 555 timer)
- 2- 2Resistnace of value 10k
- 3- 2 capacitors of 0.01  $\mu\text{F}$
- 4- ic 555 connection circuit
- 5- power of 5 - 15 volt


### **\*introduction to filtered square wave method:**

This way produce a sine wave by selecting it with a filter. The idea is to generate a square wave first. As it turns out, it's often easier to generate a square wave or rectangular wave than a sine wave. According to Fourier theory, the square wave is made up of a fundamental sine wave and an infinite number of odd harmonics.

A CMOS 555 timer IC produces a 50% duty cycle square wave. Its output is sent to a low pass RC filter that filters out the


harmonics, leaving only the fundamental sine wave. Some distortion is common as it's difficult to completely eliminate the harmonics. A more selective LC filter can be used to improve sine wave quality. Keep in mind that you can also use a selective band pass filter to pick out one of the harmonic sine waves.

### \*Design:

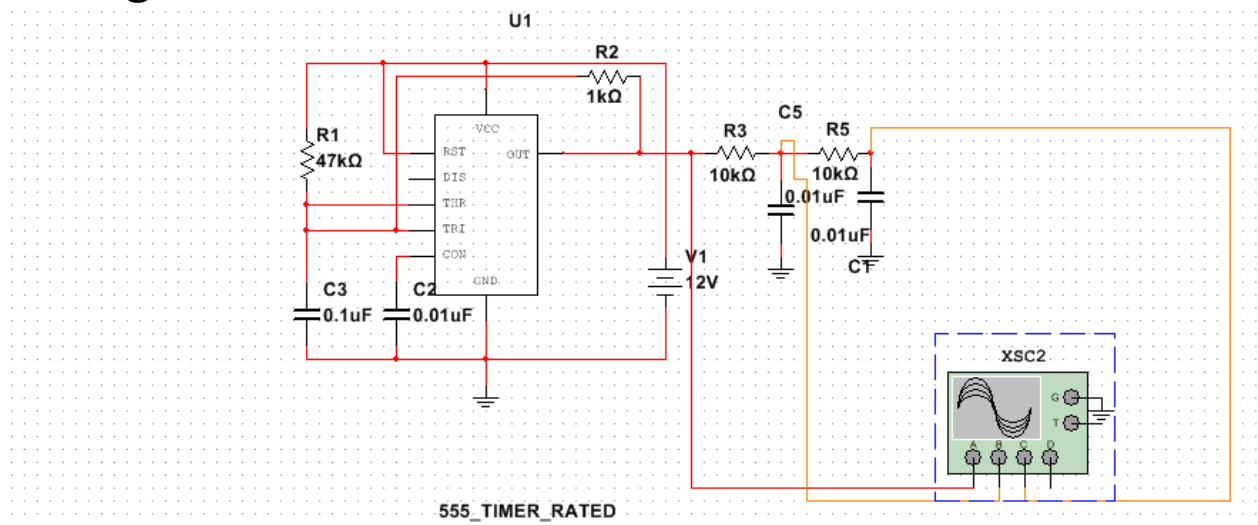
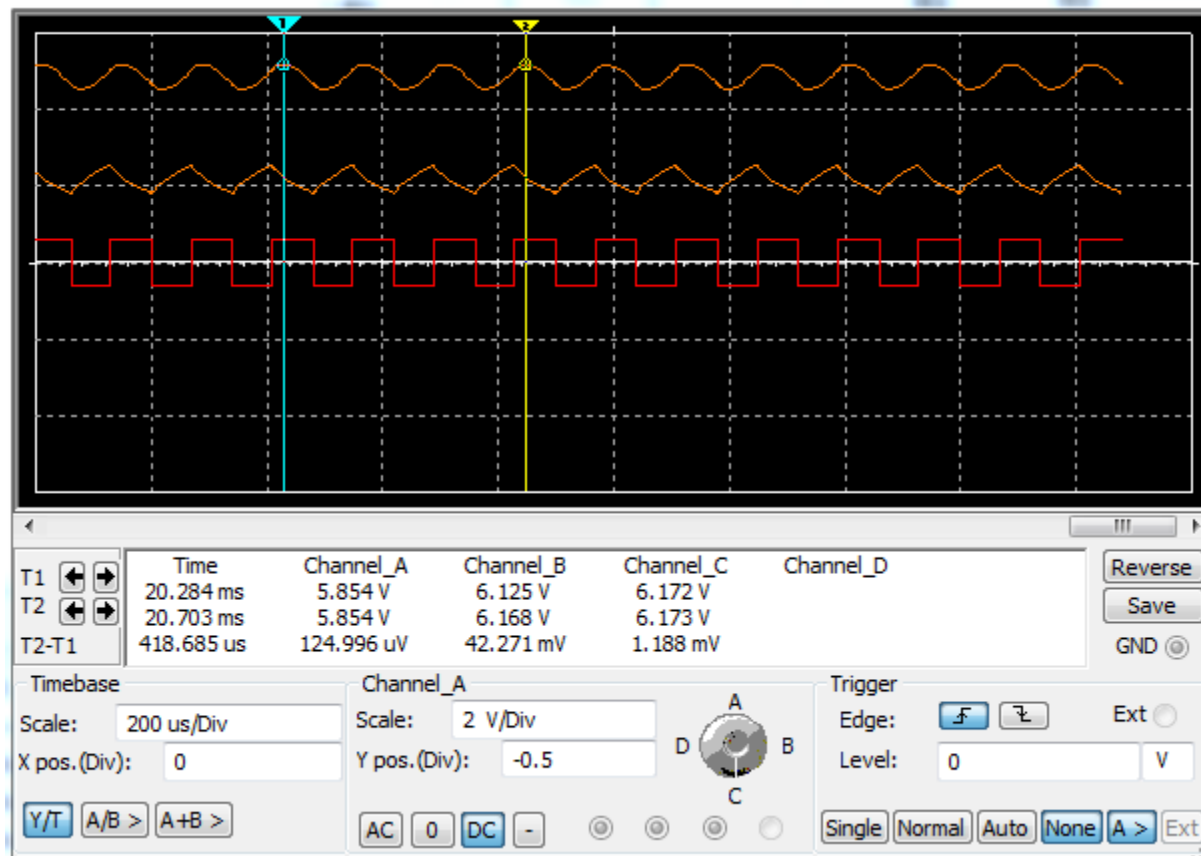
### \*idea:

For this method we connect 2 integrator circuits (consists of a resistor and a capacitor) to convert the square wave resulted from the ic 555 connection to a sine wave, as we know from the capacitor equation  $i_c = C(dV_c/dt)$  by using the first integrator circuit the square wave resulted from the ic 555 will be converted to a triangle wave then we use other integrator circuit to convert the triangle wave to a sine wave.



as we can see from the oscilloscope above is connected to the circuit with three wires each wire is connected to a converting point .

the change in the wave type can be noticed.

time constant =  $RC = 5.28 \times 10^{-6}$  sec